

ECE 10, Winter 2021, Homework #5, Due March 5, 2021

Problem 1: Refer to Figure 1 for this problem. Assume that $R_1 = 5 \text{ k}\Omega$, $R_2 = 16 \text{ }\Omega$, $L = 400 \text{ nH}$, $C = 4 \text{ nF}$, and $V_0 = 10 \text{ Volts}$. This is a continuation of Problem #6 from Homework #3 where you derived the differential equation in terms of $i(t)$, and calculated the values of $i(t)$, its first derivative, and its second derivative at time $t = 0+$. You are allowed to get all necessary information from the posted solutions to Problem #6 from Homework #3.

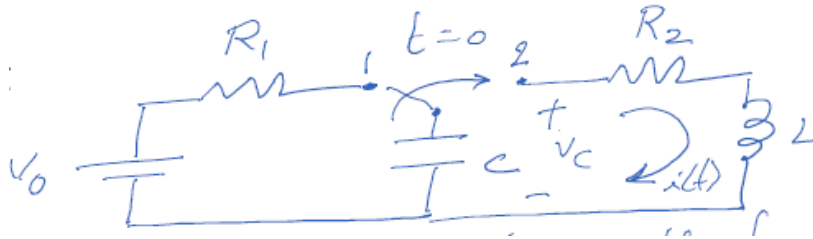


Figure 1.

- Solve the differential equation and obtain an expression for $i(t)$ for all time $t \geq 0$.
- Derive an expression for the voltage $v_C(t)$ for all time $t \geq 0$.

(10 + 5 = 15 points)

Solution:

Problem 2: Consider the circuit shown in Figure 2. Assume that $C = 0.25\text{F}$, $L = 1\text{H}$, $R = 1\text{ Ohm}$, $V_B = 1\text{V}$, $v_C(0^-) = 2\text{V}$, and $i_L(0^-) = 1\text{A}$. Find expressions for $v_C(t)$ and $i_L(t)$ for time $t \geq 0$.

(20 points)

Solution:

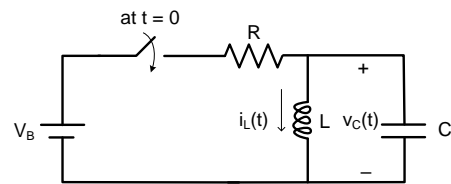


Figure 2

Problem 3: (Problem 6.15 from textbook) Assume that $V_B = 100\text{V}$, $C = 10\mu\text{F}$, $R = 10\Omega$, and $L = 1\text{H}$ in Figure 3. In the network, the switch is closed, and a steady state is reached. Subsequently, at time $t = 0$, the switch is opened. Find an expression for the current in the inductor, $i_2(t)$ for time $t \geq 0$.

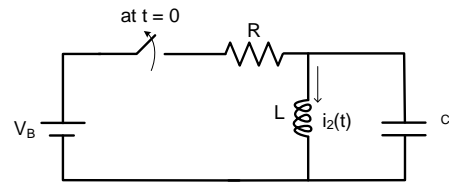


Figure 3

(10 points)

Solution:

Problem 4: Compute the phasors, if they exist, corresponding to the following signals.

a. $x(t) = -2\sin(50\pi t - 135^\circ)$

b. $x(t) = 5\sin(340\pi t + 135^\circ) - 12\cos(340\pi t - 60^\circ)$

c. $x(t) = 4\sin(400\pi t - 135^\circ) + 3\cos(4000\pi t - 60^\circ)$

(2 + 2 + 2 = 6 points)

Solution:

Problem 5: Compute the sinusoidal signals corresponding to the following phasors.

a. $\underline{X} = 4 - j3 - 12/j$, $\omega = 7$ krad/s

b. $\underline{X} = 8e^{-j5\pi/6}$, $\omega = 10$ rad/s

(2 + 2 = 4 points)

Solution:

Problem 6: Refer to the circuit schematic shown in Figure 4. Assume that $L = 2\text{nH}$, $C = 5\text{pF}$, and $R = 50\text{ Ohms}$.

(a) Find the equivalent impedance, Z , looking into 1-1' when $f = 2\text{ GHz}$.

(b) Suppose a current source, $i_B(t) = 2\cos(4\pi \times 10^9 t)$ Amperes, is applied between 1 and 1' nominally flowing into 1 and out of 1'. Using phasor analysis, calculate the phasors, \underline{V}_C , \underline{V}_X , \underline{I}_R , and \underline{I}_L , that correspond to $v_C(t)$, $v_R(t)$, $i_R(t)$, and $i_L(t)$, respectively.

(c) Draw a phasor diagram for this circuit, i.e., sketch the phasors \underline{V}_C , \underline{V}_X , \underline{I}_R , and \underline{I}_L , on a complex plane

(d) Derive expressions for the steady state time-domain signals, $v_C(t)$, $v_R(t)$, $i_R(t)$, and $i_L(t)$.

(10 + 15 + 4 + 6 = 35 points)

Solution:

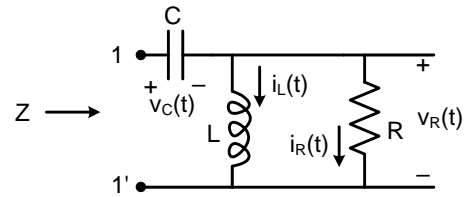


Figure 4.

